



## CS232 : Digital Logic Design and Computer Architecture

### Lab 1 (10 points)

#### Setup Instructions:

1. Download roll\_number.zip from [drive](#) and unzip it, enter the Digital folder
2. Execute `bash Digital.sh` to start the application
3. **Please go through the tutorial triggered to learn how to build a circuit**

**Tip:** For each component, hover over the pins to know the usage


**Tip2:** For a component, right clicking allows you to change its parameters

#### Q1 (2 points):

1. Create a combinatorial circuit to map the output of the 2-bit counter to the control pins of the 7-edge display
  - a. replace the 2bitdisplay\_component with your combinatorial circuit
  - b. construct the other components i.e, input, clock, counter and display as shown in the

## CS232 : Digital Logic Design and Computer Architecture Lab

Updated automatically every 5 minutes

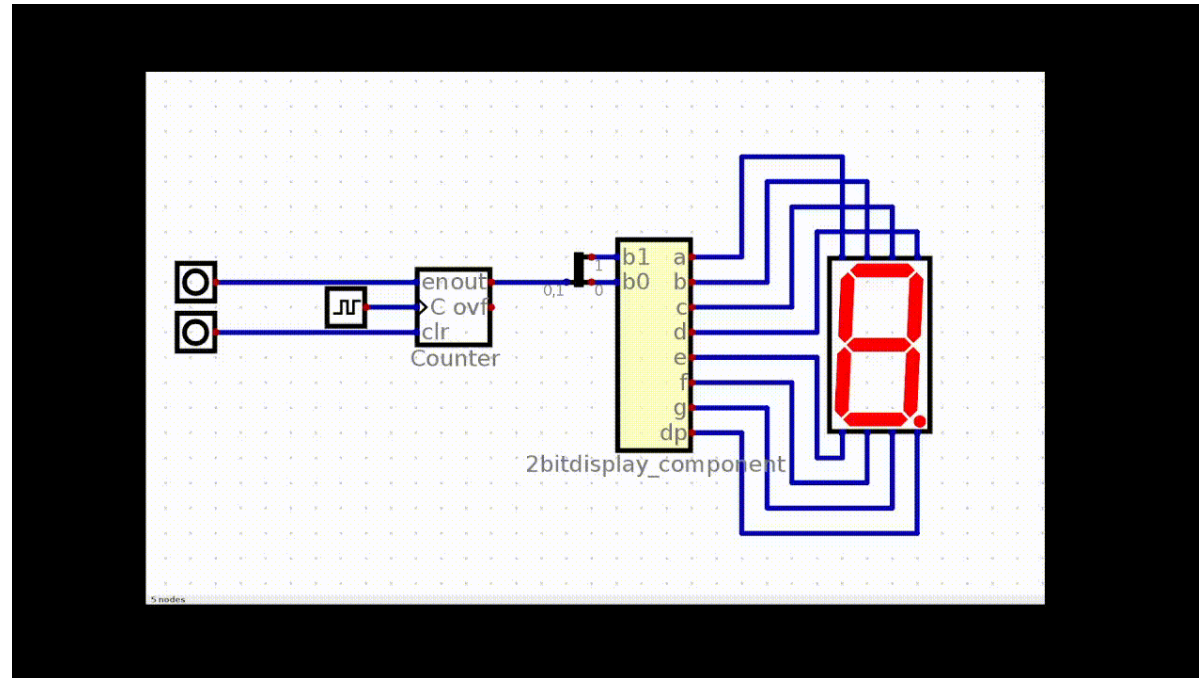

## Grading Policy:

- 2 points for a complete working solution
- 0 points for the rest

**Q2 (3 points):**

1. Create a 2-bit up down counter using D-Flip flops. A 2-bit up-down counter's output varies as given: 0->1->2->3->2->1->0 and repeat.
2. You are allowed to use at most 3 D-Flip flops and NOT gate along with any 2-input logic gates


## CS232 : Digital Logic Design and Computer Architecture Lab

Updated automatically every 5 minutes

- 0 points for the test

**Q3 (5 points):**

1. Implement a traffic light system which pauses for 2 seconds on red light, 1 second on yellow light and 2 seconds on green light.
2. You are again allowed to use at most 3 D-Flip flops, and NOT gate along with 2-input logic gates and LED components (under IO section).
3. Save the final file as q3.dig

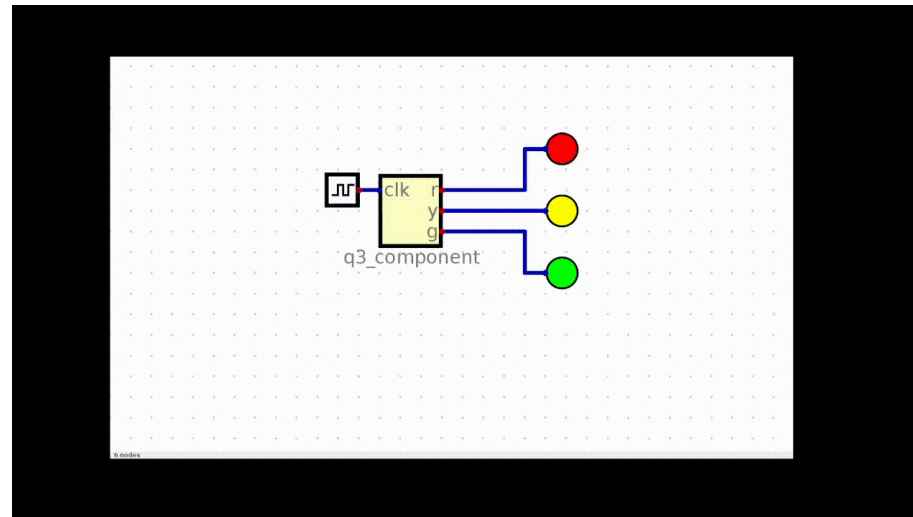**Grading Policy:**

- Full 5 point for < 5 gates used
- 3 points for any working solution
- 0 for any other case



Published using Google Docs

[Learn more](#)[Report Abuse](#)

---

CS232 : Digital Logic Design and Computer Architecture LabUpdated automatically every 5 minutes

---

`roll_number.zip` `roll_number` and submit  
`roll_number.zip` on moodle.

**Incorrect submission formats will result in no marks.**

**Note:** Replace `roll_number` used throughout with your  
roll number.

**Late submission policies:**

1. -10% for each day of late submission